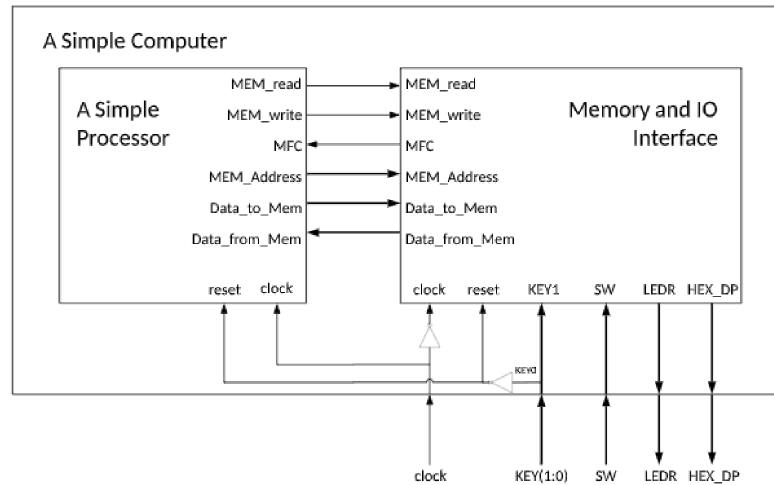


CSCE 230 – Group Labs (the Project)

5. Computer organization

5.1. A simple computer consists of a simple processor and a memory and IO interface.



5.2. VHDL designs

- A Simple Computer: SimpleComputer.vhd, which is complete and is the **top-level entity** for Quartus.
- A Simple Processor: SimpleProcessor.vhd. which is **incomplete** and is what you need to complete in this project.
- Memory and I/O:
 - MemoryIOInterface.vhd, which is complete.
 - MainMemory.vhd, which is complete.
 - MemoryInitialization.mif, which is **incomplete** and is where you need to write the binary/hexadecimal encodings of an assembly program. This mif file will be automatically read by MainMemory.vhd to initialize the initial values of memory.

5.3. Computer Interface




- The processor clock input port is directly connected to the computer clock input port, and is triggered by a rising edge of the computer clock. The memory and IO clock input port is connected to the output of a NOT gate, and thus is triggered by a falling edge of the computer clock.
- When KEY0 is pushed (i.e. KEY0=0), the computer is reset. Therefore, the inverted KEY0 is connected to the reset input ports of the processor and memory and IO interface.

5.4. Main memory and I/O ports

Base Address	End Address	Memory or I/O	16-bit data at an address
0x0000	0x0FFF	Main memory	
0x1000	0x1000	LEDR: LED Red (Write only)	000000:LEDR9:LEDR8:....:LEDR0
0x1010	0x1010	HEX_DP: Hex Seg (Write only)	00000000:HEX57:HEX47:....:HEX07
0x1040	0x1040	SW: Slider Switch (Read only)	000000:SW9:SW8:....:SW0
0x1050	0x1050	KEY: Push Button (Read only)	000000000000:KEY1:0

in
out

Data-R4

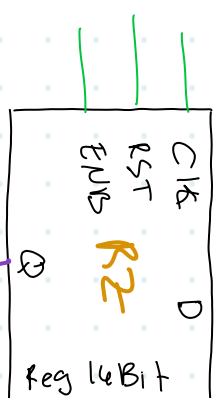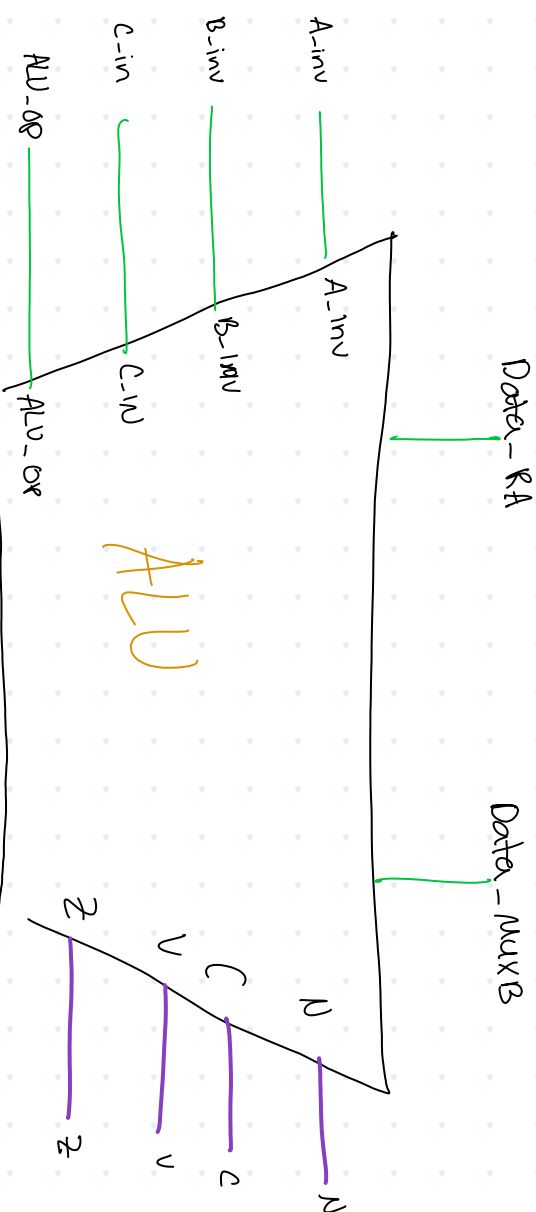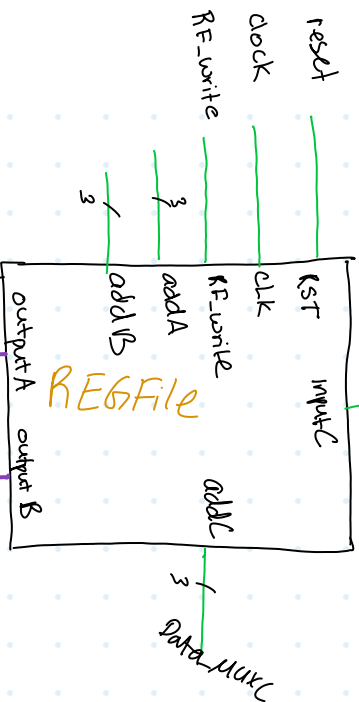


Data-RB



Data-Extension

Data-RB
Data-RM

Data-MuxY

Data-RZ-MuxMA



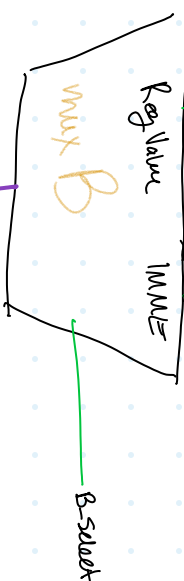


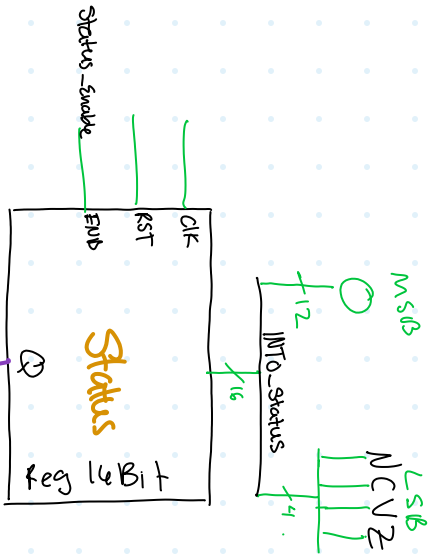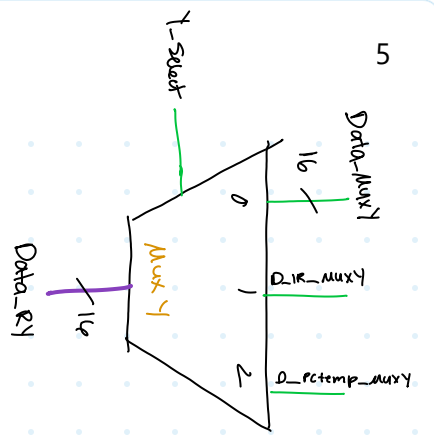

Data = RM




Data-Mem-ID

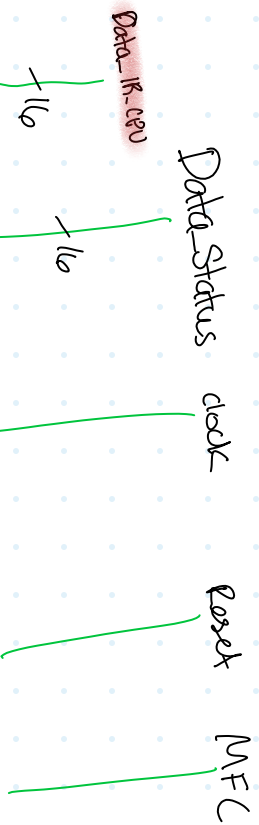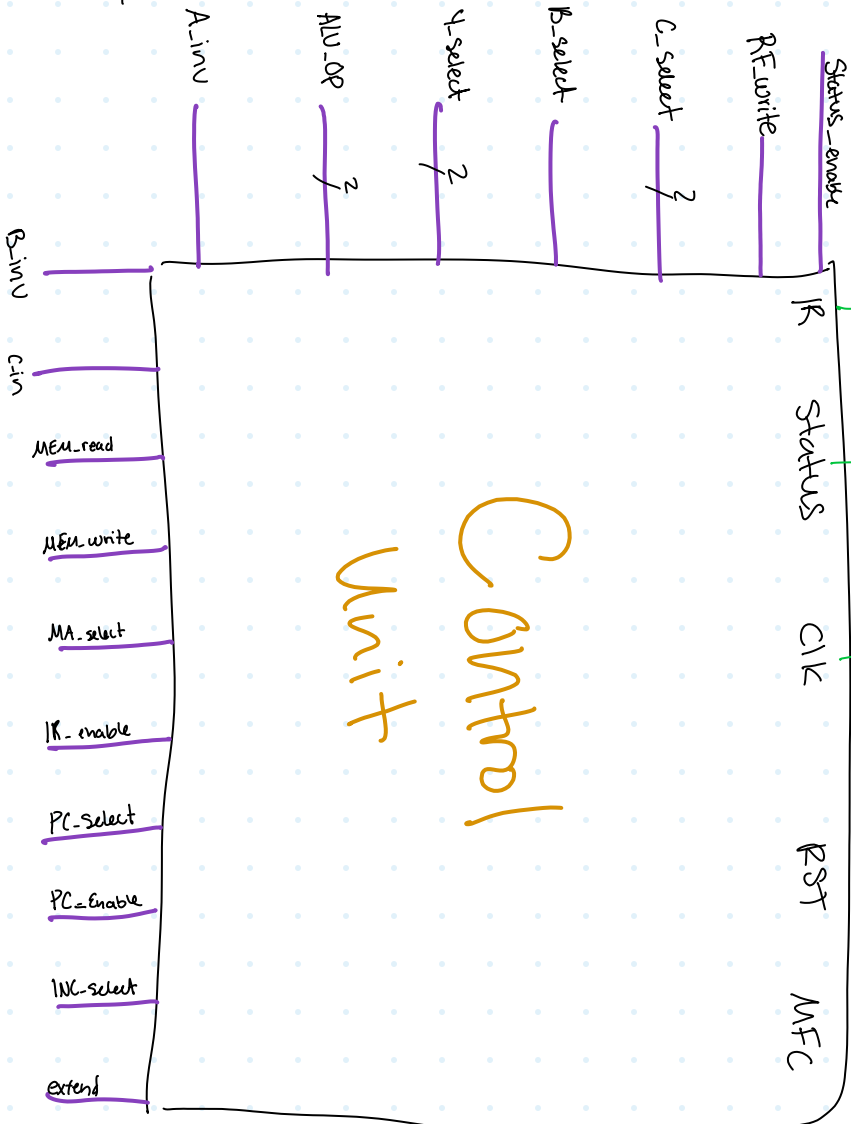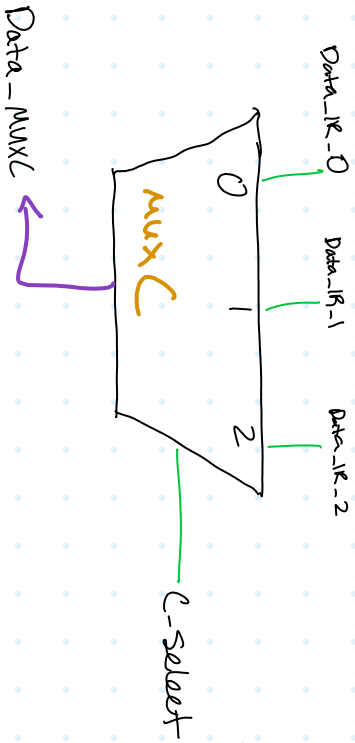


RST

MFC

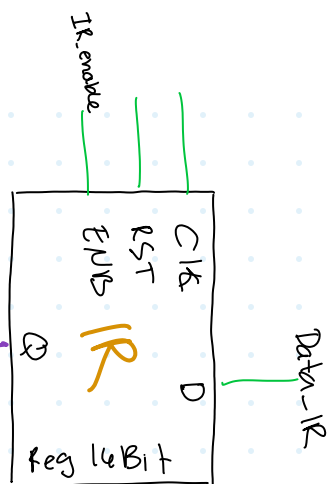

Data-IR-CPU



Data-IR-IMME

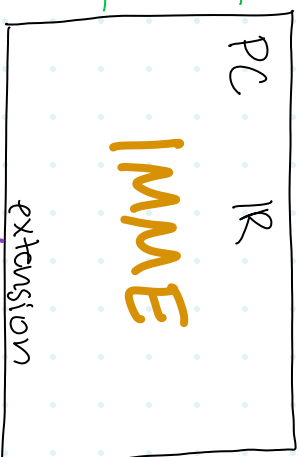

Data-Extension

Data-Exten-MuxRc

Data-Exten-MuxIMC

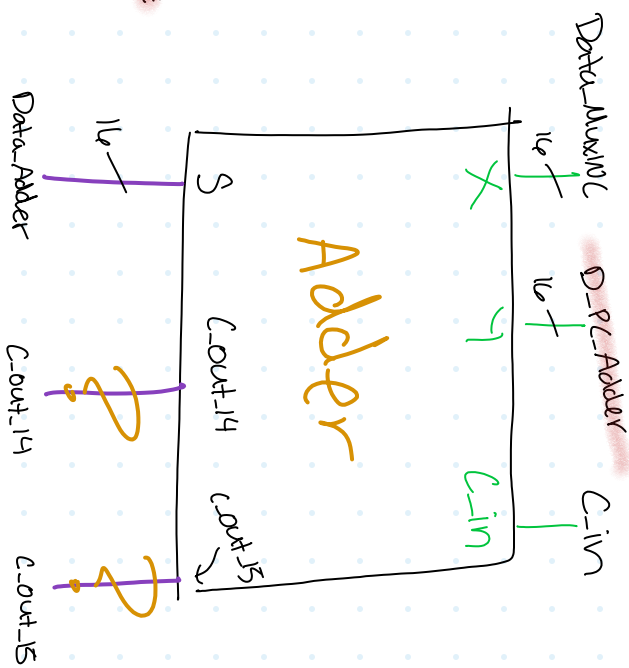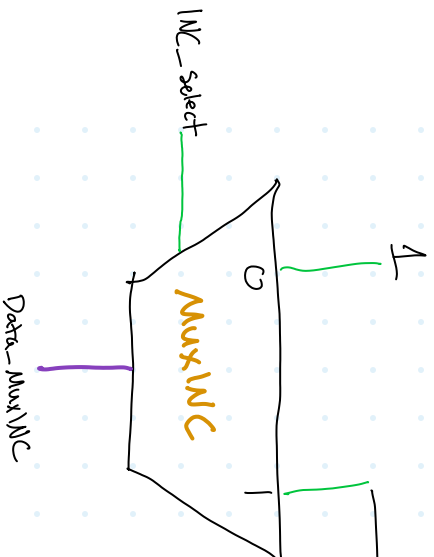

Data-Adder

C-out-14

C-out-15

D-PC-IMME

D-PC-Adder

Data-PC-MuxIMC

Data-PC-stmp

Data-RZ-MuxIMC

